

**Government College of Engineering, Amravati**  
(An Autonomous Institute of Government of Maharashtra)

**Third Semester B. Tech. (Instrumentation Engineering)**

**Winter – 2016**

**Course Code: INU302**

**Course Name: Electronics Devices and Circuits**

**Time: 2 hr.30min.**

**Max. Marks: 60**

**Instructions to Candidate**


- 1) All questions are compulsory.
- 2) Assume suitable data wherever necessary and clearly state the assumptions made.
- 3) Diagrams/sketches should be given wherever necessary.
- 4) Use of logarithmic table, drawing instruments and non-programmable calculators is permitted.
- 5) Figures to the right indicate full marks.

**1**

**Solve ANY TWO from following questions.**

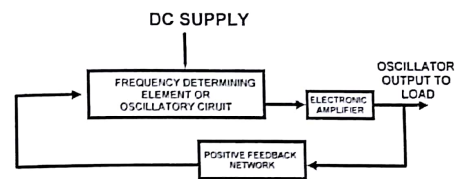- (a) Derive an expression for ripple factor of a full wave rectifier with LC filter. **6m**
- (b) Explain the working of positive and negative clipper. What are the applications of clipper? **6m**
- (c) Explain working principle of (i) Zener diode (ii) Tunnel diode. Give their characteristics and typical applications. **6m**

- 2 **Solve ANY TWO from the following questions.** 6m
- (a) Draw the various operating regions of a common emitter transistor on its output characteristics and explain it. 6m
- (b) Define the three different stability factors and give an expression that determines the variation of collector current in terms of stability factor? 6m
- (c) Discuss analysis of transistor amplifier using h-parameter in CE configuration. 6m
- 3 **Solve the following questions.**
- (a) For a series fed class A large signal amplifiers draw the output characteristics and current and voltage waveforms. Derive expression for output power. 6m
- (b) Discuss the general characteristics of feedback amplifier in detail. 6m
- 4 **Solve ANY TWO from following questions.**
- (a) Draw the circuit diagram of an astable multivibrator. Justify that it is a two stage RC coupled amplifier using feedback. How does it generate a square wave? 6m
- (b) A block diagram of an oscillator is shown in figure; discuss the use of each block. Design one of the oscillators and explain it. 6m



- (c) What are the two basic conditions for oscillation? 6m  
Design colpitt's oscillator and also give its frequency of oscillation?
- 5 **Solve the following questions.**
- (a) Distinguish between BJT and FET in detail. What is the difference between FET and MOSFET? 6m
- (b) Draw the characteristics of FET and derive an expression for pinch-off voltage and saturation drain current. 6m