

GOVERNMENT COLLEGE OF ENGINEERING AMRAVATI
(An Autonomous Institute of Government of Maharashtra)
Department of Electronics and Telecommunication
Class Test II

Subject: ETU 501 Linear Integrated Circuits and Applications

Date: 19/09/2016

Marks: 15

SOLVE ANY THREE

- Q1. Design a first order low pass Butterworth filter at a cut-off frequency of 2 KHz with pass band gain of 4. Plot the frequency response for this filter. Using frequency scaling technique convert the cut-off frequency of 2 KHz to 3.2 KHz. (5M)
- Q2. What is frequency response; explain with the help of high frequency model of OP-AMP. Write observations made from same frequency response. (5 M)
- Q3. Explain the need of frequency compensation. What is difference between compensated and non-compensated op-amp. (5 M)
- Q4. Explain Pole-zero compensation technique. (5 M)

Winter 2019

Date: 25/9/2019

Semester: V

CT-2 EXAMINATION

Time: 1 Hr

Course: ETU501LIC

Marks:15

Q1) Solve the following questions

A) The output voltage V_o of the circuit as shown in the figure 1, is given by expression $A_1 V_1 + A_2 V_2$. Where V_1 and V_2 are input voltages. Assuming ideal op-amp, find A_1 and A_2 .
OR
B) For the circuit shown in Fig. Q.2, show that-

- $A_d = 1 + (R_f/R_1)$
- $R_{in1} \neq R_{in2}$

What is a drawback of this circuit? Suggest suitable circuit that overcomes the drawback.

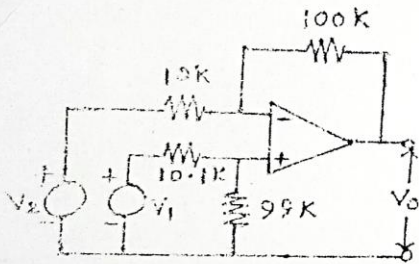


fig 1

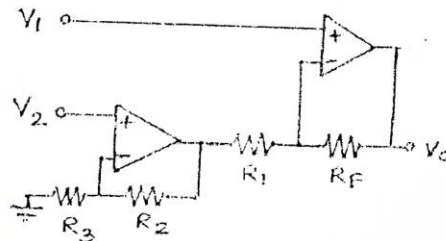


Fig.2

C) (i) Write short note on "Bridge Amplifier"

(ii) Draw the waveform of input and output signal if $600\mu V$ peak to peak triangular wave signal is applied at the input of an open loop op amp having gain = $100dB$. Assume 100% output voltage swing.

4M

D) Draw a differential amplifier using an ideal op-amp. And derive the expression for the output voltage.

4M

E) State limitations of instrumentation amplifier using two op amps. How these limitations can be overcome?

4M