

**Government College of Engineering, Amravati**  
(An Autonomous Institute of Government of Maharashtra)

**Sixth Semester B. Tech.**  
**(Computer Science and Engineering)**

**Summer – 2016**

**Course Code: Switching Theory and Logic Design**

**Course Name: CSU601**

**Time: 2 Hrs. 30 Min.**

**Max. Marks: 60**

**Instructions to Candidate**

- 1) All questions are compulsory.
- 2) Assume suitable data wherever necessary and clearly state the assumptions made.
- 3) Diagrams/sketches should be given wherever necessary.
- 4) Use of logarithmic table, drawing instruments and non-programmable calculators is permitted.
- 5) Figures to the right indicate full marks.

**1. Solve any two:**

- (a) Show type classification available in VHDL and explain scalar data type in brief. 6m
- (b) Explain case, wait and loop sequential statements in detail with example. 6m
- (c) Design VHDL code for 9 bit parity generator circuit 6m

**2. Solve:**

- (a) Write short note on: 4m
  - i) Explicit visibility with clauses
  - ii) Operator overloading

- (b) Write VHDL code for: 8m  
i) 1bit full adder using dataflow modeling  
ii) synchronous D-type flip-flop triggered on the rising edge of the clock signal using behavioural modelling

3. **Solve:**

- (a) Simplify the following Boolean function: 4m  
 $F(A,B,C,D) = \Sigma_m(1,2,4,7,8,11,13,14)$

- (b) Find all the prime implicants for the Boolean functions given and determine which are essential PI  $F(A,B,C,D) = \Sigma_m(0,1,3,4,5,7,13,15)$ , using Tabulation method 6m

- (c) Prove that the compliment of a function is equal to complementing a function using dual method. 2m

4. **Solve any one:**

- (a) Design BCD to 7 segment LED code convertor. 12m

- (b) (i) Design BCD to Excess-3 code convertor 6m

- (ii) Design VHDL code for 3:8 decoder using Data flow modeling and logic circuit along with its truth table 6m

5. **Solve**

- (a) Design 3 bit synchronous up counter using J-K flip flop. 6m

- (b) What are shift register? Explain bi-directional shift register with parallel load in detail 6m

**Government College of Engineering, Amravati**  
(An Autonomous Institute of Government of Maharashtra)

**Sixth Semester B. Tech. (Computer Science & Engg.)**

**Summer– 2017**

**Course Code: Switching Theory & Logic Design**

**Course Name: CSU601**

**Time: 2 Hrs. 30 Min.**

**Max. Marks: 60**

**Instructions to Candidate**

- 1) All questions are compulsory.
- 2) Assume suitable data wherever necessary and clearly state the assumptions made.
- 3) Diagrams/sketches should be given wherever necessary.
- 4) Use of logarithmic table, drawing instruments and non-programmable calculators is permitted.
- 5) Figures to the right indicate full marks.

1. Solve any two:
  - (a) Explain the following sequential statements: if, case, null and exit. 6m
  - (b) Design VHDL code for 9 bit parity generator circuit 6m
  - (c) What are signal assignment statements? Elaborate them in detail. 6m
2. Solve:
  - (a) Write down VHDL code for given circuits: 6m
    - i) 1 bit full adder using mixed modeling.
    - ii) 2:4 decoder using behavioural modeling.

*Contd..*



- (b) Write short note on: 6m
- i) Functions
  - ii) Overloading & Visibility
  - iii) Use clause & Generic constants.

3. Solve:

- (a) Simplify the following Boolean function: 6m
- i)  $F(w,x,y,z) = \sum_m(0,1,2,4,5,8,10,12,14)$
  - ii)  $F(a,b,c,d) = \sum_m(0,2,6,8,12,13,15) + d_m(3,4,9)$

- (b) Minimize the given logic function using 6m  
Tabulation method and determine Prime  
implicants & essential PI,  
 $F(A,B,C,D) = \sum_m(0,1,2,3,5,7,8,10,12,13,15)$


4. Solve any two:

- (a) Design BCD to Excess-3 code convertor 6m
- (b) Explain Adders in detail with its types and 6m  
implementation.

- (c) Consider the combinational circuit shown below: 6m
- i) Derive the Boolean expressions for  $T_1$  through  $T_4$ . Evaluate the outputs of  $F_1$  and  $F_2$  as a function of the four inputs.
  - ii) List the truth table with 16 binary combinations of the four inputs variables. Then list the binary values for  $T_1$  through  $T_4$  and outputs  $F_1$  and  $F_2$  in the table.
  - iii) Plot the output Boolean functions obtained in part (i) on maps and show that the simplified Boolean expressions are equivalent to the ones obtained in part (a).

5.

 - (a) Solve  
Design  
flip
- (b) Explain  
as it
- (c) What  
brief



5.

(a) Solve any two:

Design 3 bit synchronous down counter using T flip flop.

6m

(b)

Explain synchronous counters with BCD counter as its type.

6m

(c)

What are shift register? Explain serial transfer in brief with example.

6m