

**Government College of Engineering, Amravati**  
(An Autonomous Institute of Government of Maharashtra)

**Third Semester B. Tech. (Instrumentation Engineering)**

**Winter – 2016**

**Course Code: INU305**

**Course Name: Digital Electronics**

**Time: 2 Hrs. 30 Min.**

**Max. Marks: 60**

**Instructions to Candidate**

- 1) All questions are compulsory; solve any two sub-questions from Q1, Q2 and Q3.
- 2) Assume suitable data wherever necessary and clearly state the assumptions made.
- 3) Diagrams/sketches should be given wherever necessary.
- 4) Use of logarithmic table, drawing instruments and non-programmable calculators is permitted.
- 5) Figures to the right indicate full marks.

**Q1 A** Describe the ways of representing negative numbers in binary. Why 2's complement method is preferred more for signed number representation? **6M**

**B** Describe the Gray's Code, enlist their properties and importance and explain BCD to Gray's code convertor. **6M**

**C** Perform following subtraction using 9's and 10's complement methods; Why complemented addition is performed instead of subtraction?  
(786-538.85)<sub>10</sub> **6M**

**Q2 A** Simplify the given function using Quine-McCluskey method and verify the result using K-maps. **6M**  
 $Y(A,B,C,D,E) = \sum m\{0,2,5,7,13,15,18,20,23,28,31\} + d(21,29)$

- B Convert the following standard SOP form expression to equivalent reduced SOP form, reduced POS form and Standard POS form expressions 6M  

$$Y = \bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC$$
- C What is the need of look ahead carry generator circuit? Design the same suitable for four bit *parallel addition*. 6M
- Q3 A Design a 1-bit magnitude comparator. Draw and explain logic circuit of 5 bit magnitude comparator using minimum number of IC7485 ICs. 6M
- B Describe the working of Master-Slave JK flip-flop mentioning its importance. 6M
- C What are the types of Shift Registers? Describe a shift register having facility of parallel loading and shifting along with parallel outputs. 6M
- Q4 A What are the types of Digital to Analog(D/A) convertor? Describe R-2-R ladder and define the term resolution concern with D/A conversion. 6M
- B Describe the following semiconductor memories 6M  
 a. CCD      b. Flash Memory      c. RAM Cell
- Q5 A Describe field programmable gate array (FPGA)? Explain the configurable logic blocks with necessary block diagram. 6M
- B Describe following characteristics of digital ICs: 6M  
 i. Fan-in ii. Fan-out (2M)  
 iii. Propagation delay iv. Noise Margin (4M)